

*Presentation Topic:*

**ANALOG TO DIGITAL CONVERSION  
(ADC)**



# ADC Basic Principle:

- The basic principle of operation is to use the comparator principle to determine whether or not to turn on a particular bit of the binary number output.
- It is typical for an ADC to use a digital-to-analog converter (DAC) to determine one of the inputs to the comparator.



## 3 Basic Types


- Flash ADC
- Digital-Ramp/Dual slope/Counter slope ADC
- Successive Approximation ADC



## 1-> Flash ADC

- Consists of a series of comparators, each one comparing the input signal to a unique reference voltage.
- The comparator outputs connect to the inputs of a priority encoder circuit, which produces a binary output

# 3 bit Flash ADC Circuit

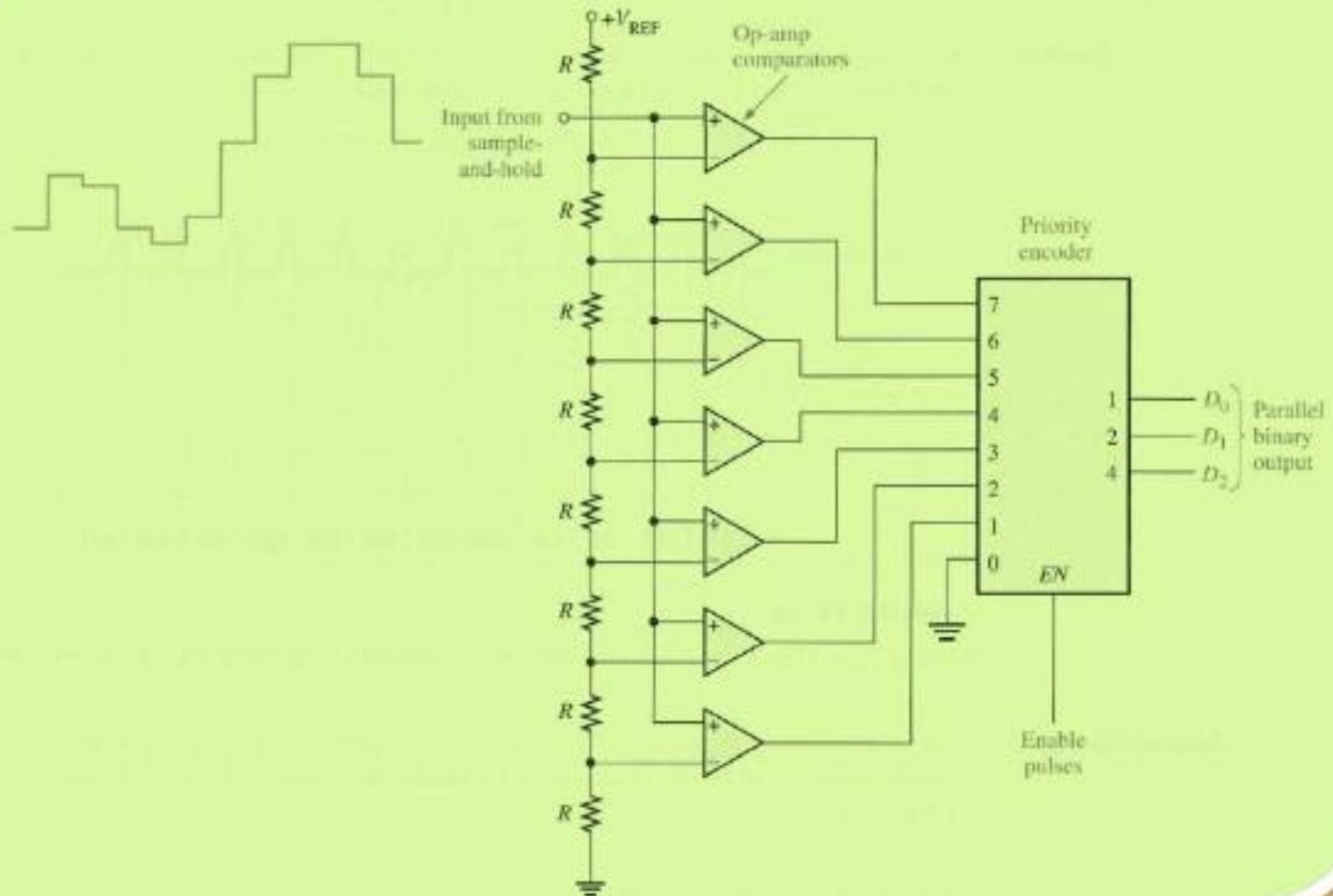



# How Flash Works

- As the analog input voltage exceeds the reference voltage at each comparator, the comparator outputs will sequentially saturate to a high state.
- The priority encoder generates a binary number based on the highest-order active input, ignoring all other active inputs.



# Flash

## Advantages

- Simplest in terms of operational theory
- Most efficient in terms of speed, very fast  
limited only in terms of comparator and gate propagation delays

## Disadvantages

- Lower resolution
- Expensive
- For each additional output bit, the number of comparators is doubled  
i.e. for 8 bits, 256 comparators needed


2->

## Dual Slope ADC

- Also known as Counter-Ramp or Digital Ramp ADC
- A dual slope ADC is commonly used in measurement instruments (such as DVM's).



# Dual Slope ADC circuit

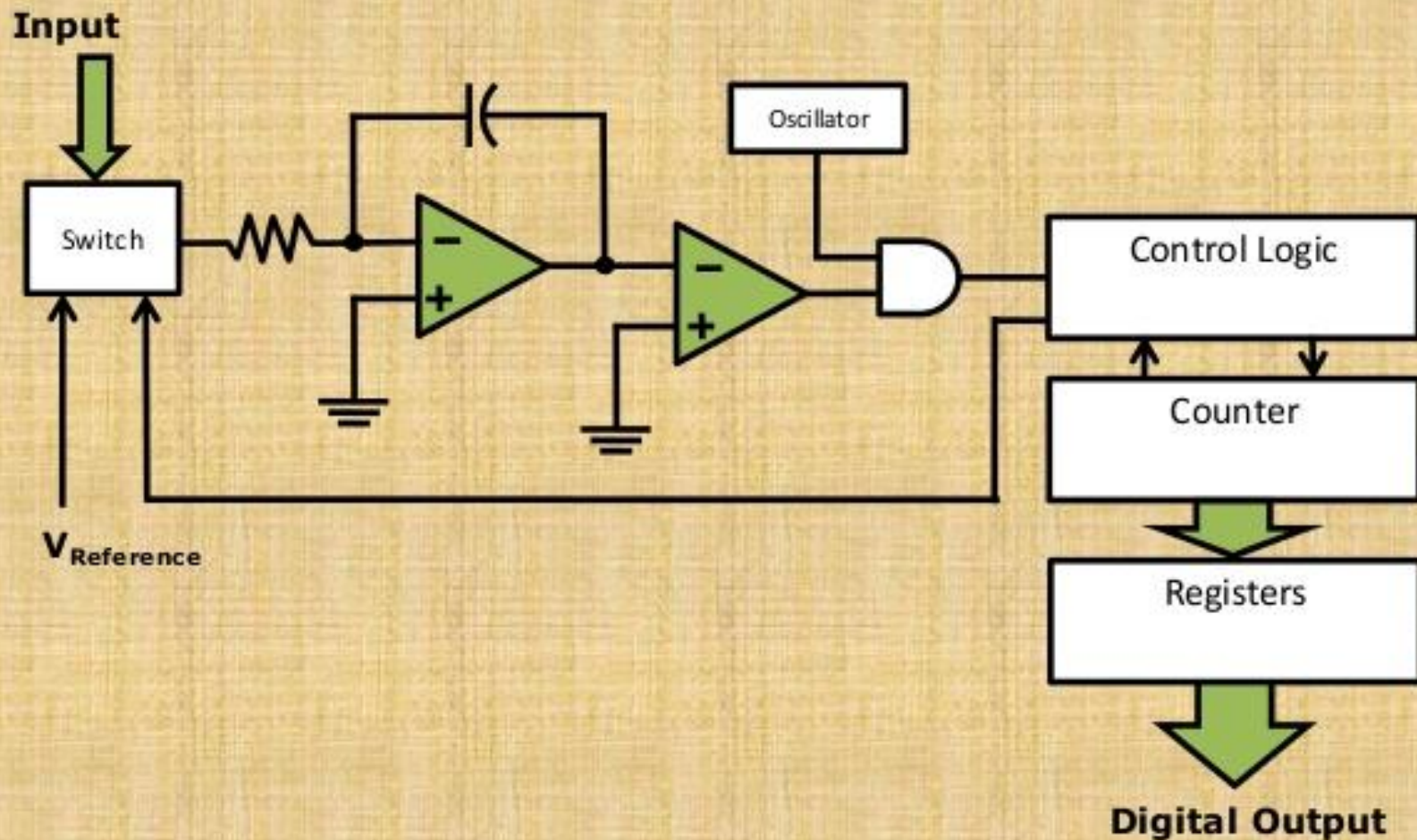




# Dual Slope Function

- The Dual Slope ADC functions in this manner:
  - When an analog value is applied the capacitor begins to charge in a linear manner and the oscillator passes to the counter.
  - The counter continues to count until it reaches a predetermined value. Once this value is reached the count stops and the counter is reset. The control logic switches the input to the first comparator to a reference voltage, providing a discharge path for the capacitor.
  - As the capacitor discharges the counter counts.
  - When the capacitor voltage reaches the reference voltage the count stops and the value is stored in the register.


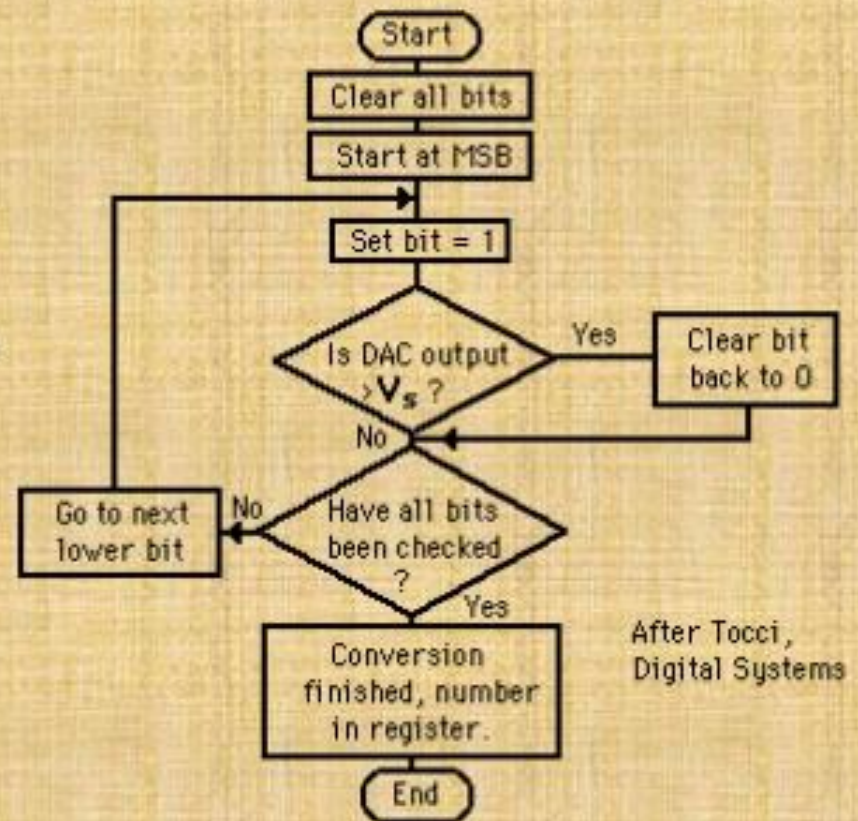
# Successive approximation ADC

- Much faster than the digital ramp ADC because it uses digital logic to converge on the value closest to the input voltage.
- A comparator and a DAC are used in the process.






# Successive Approximation ADC

- A Successive Approximation Register (SAR) is added to the circuit
- Instead of counting up in binary sequence, this register counts by trying all values of bits starting with the MSB and finishing at the LSB.
- The register monitors the comparators output to see if the binary count is greater or less than the analog signal input and adjusts the bits accordingly



# Successive Approximation ADC Circuit

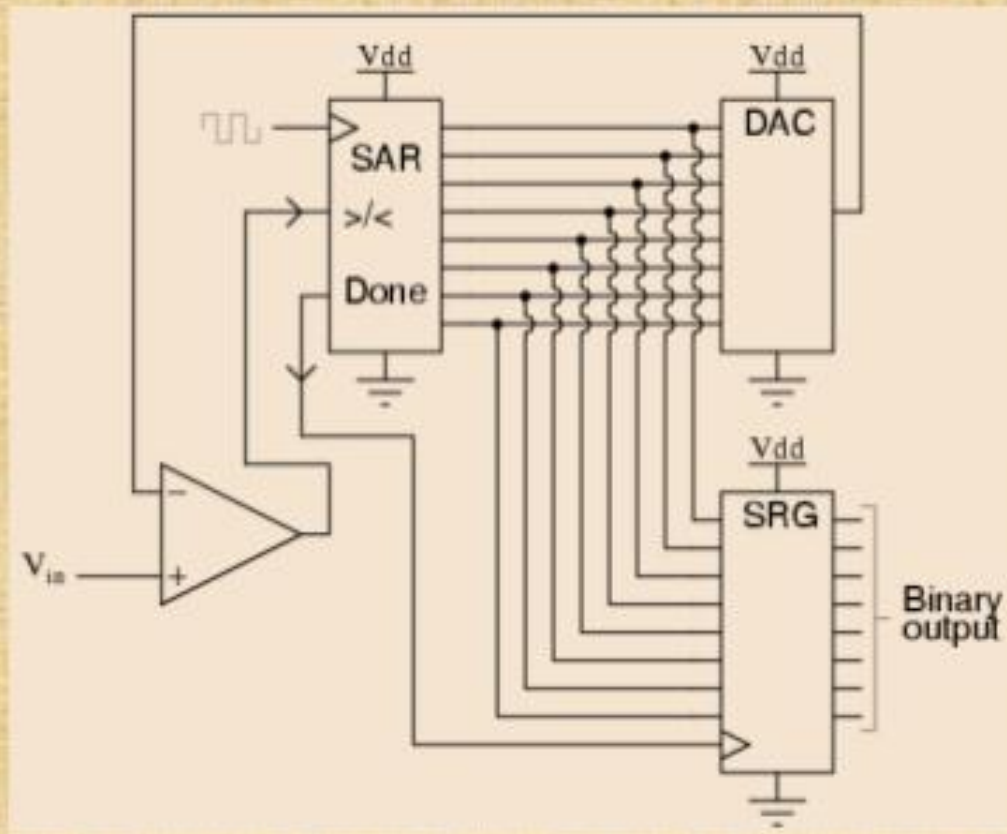

# Examples of A/D Applications

- **Microphones** - take your voice varying pressure waves in the air and convert them into varying electrical signals
- **Strain Gages** - determines the amount of strain (change in dimensions) when a stress is applied
- **Thermocouple** — temperature measuring device converts thermal energy to electric energy
- **Voltmeters**
- **Digital Multimeters**